

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020
Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the construction, working and characteristics of photo diode. (06 Marks)
- b. With hysteresis characteristics explain the working of Schmitt trigger circuit (Inverting). (06 Marks)
- c. With a neat circuit diagram and mathematical analysis explain voltage divider bias circuit. (08 Marks)

OR

- 2 a. Explain the working of R-2R ladder D to A converter. (06 Marks)
- b. Explain successive approximation A to D converter. (06 Marks)
- c. Show how IC-555 timer can be used as an astable multivibrator. (08 Marks)

Module-2

- 3 a. Find the minimum SOP and minimum POS expressions for the following function using K-map. $f(A, B, C, D) = \sum_m(1, 3, 4, 11) + \sum_d(2, 7, 8, 12, 14, 15)$. (06 Marks)
- b. What are the disadvantages of K-map method? How they are overcome in Quine Mccluskey method. Simplify following function using Q-M method $f(A, B, C, D) = \sum_m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$. (08 Marks)
- c. What is Map Entered Variable method? Using MEV method simplify following function: $f(A, B, C, D) = \sum_m(2, 3, 4, 5, 13, 15) + \sum_d(8, 10, 11)$. (06 Marks)

OR

- 4 a. With the help of flow chart explain how to determine minimum sum of products using Karnaugh map. (06 Marks)
- b. Using Q-M method simplify the following function $F(A, B, C, D) = \sum_m(2, 3, 7, 9, 11, 13) + \sum_d(1, 10, 15)$. (08 Marks)
- c. With example explain Petrik's method. (06 Marks)

Module-3

- 5 a. What are hazards in digital circuits? Explain different types of hazards. (06 Marks)
- b. Implement full subtractor using 3 to 8 decoder and NAND gates. (06 Marks)
- c. Differentiate between PAL and PLA. Realize following functions using PLA. Give PLA table and internal connection diagram for the PLA (Use as many common terms as possible) $F_1(1, b, c, d) = \sum_m(1, 2, 4, 5, 6, 8, 10, 12, 14)$
 $F_2(a, b, c, d) = \sum_m(2, 4, 6, 8, 10, 11, 12, 14, 15)$ (08 Marks)

OR

- 6 a. What is Multiplexer? Implement following function using 8:1 MUX $f(A, B, C, D) = \sum_m(1, 2, 5, 6, 9, 12)$ (08 Marks)
- b. Design Hexadecimal (Binary) to ASCII Code Converter using suitable ROM. Give the connection diagram of ROM. (06 Marks)
- c. Explain Simulation and testing of digital circuits. (06 Marks)

1 of 2

Important Note: 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and for equations written eg. 42+8=50 will be treated as malpractice.

18CS33

Module-4

- 7 a. Explain the structure of VHDL program. Write VHDL code for 4 bit parallel adder using full adder as component. (08 Marks)
- b. Explain the working of SR latch using NOR gates. Show how SR latch can be used for switch debouncing. (07 Marks)
- c. Differentiate between Latch and Flip Flop. Show how SR flipflop can be converted to D flip flop. (05 Marks)

OR

- 8 a. Derive the characteristics equations for D, T, SR and JK flipflops. (08 Marks)
- b. Draw the logic diagram of master slave JK flipflop using NAND gates and explain the working with suitable timing diagram. (07 Marks)
- c. With example explain the syntax of conditional signal assignment statement in VHDL. (05 Marks)

Module-5

- 9 a. What is shift register? Explain the working of 8 bit SISO shift register using SR flip flop. (06 Marks)
- b. With the help of state graph, state and transition tables and timing diagram explain sequential parity checker. (06 Marks)
- c. Design a random counter using T flip flops whose transition graph is shown in Fig.Q.9(c). (08 Marks)



Fig.Q.9(c)

OR

- 10 a. What is register? Explain how 4 bit register with data, load, clear and clock input is constructed using D flip flops. (06 Marks)
- b. With a block diagram explain the working of n-bit parallel adder with accumulator. (06 Marks)
- c. Differentiate between Moore and Melay machines. Analyze following Moore sequential circuit for an input sequence of X = 01101 and draw the timing diagram. (08 Marks)

 


Fig.Q.10(c)

2 of 2

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain construction and working principle of operations of n-channel D-MOSFET along with its drain and trans-conductance characteristics. (10 Marks)
- b. Write the difference between JFET's and MOSFET's. (05 Marks)
- c. For a given self-bias configuration in Fig.Q.1(c), determine: i) I_{ds} and $V_{gs'eq}$ ii) V_{ds} and V_D . (05 Marks)

 


Fig.Q.1(c)

- 2 a. List of difference between ideal and practical op-amp amplifier. (06 Marks)
- b. With a neat diagram and waveform explain astable multivibrator using 555 timers. (07 Marks)
- c. With neat diagram and waveform explain the working of relaxation oscillation oscillator. (07 Marks)

Module-2

- 3 a. Explain positive and negative logic. List the equivalence between them. (08 Marks)
 - b. Find the minimal SOP form for the given min-terms using K-map. (06 Marks)
- $$F(A, B, C, D) = \sum m(4, 5, 6) + d(10, 12, 13, 14, 15).$$
- c. Find the minimal POS form for the given MAX-TERM using K-map (06 Marks)
- $$f(a, b, c, d) = \pi M(5, 7, 8, 9, 12) + d(0, 6, 10, 15).$$

OR

- 4 a. Using Quine-Mc-Clusky method simplify the following Boolean equation. (10 Marks)
- $$f(a, b, c, d) = \sum m(0, 1, 10, 11, 13, 15) + d(2, 3, 12, 14).$$
- b. Define Hazard. Explain different types of Hazards. (06 Marks)
 - c. Write the VHDL code for the circuit shown in Fig.Q.4(c): (04 Marks)

 


Fig.Q.4(c)